

1) Draw a circuit to measure the potential difference across a filament lamp?

2) How does a step-down transformer work?

3) Draw the current-voltage graph for a filament lamp.

4) Compare alpha and beta radiations.

5) A heater has a power input of 1500 watts. The useful power output is 625 watts for this heater. Calculate the efficiency of this heater.